

LAB 4 Report

Name: Aryan Agarwal

UT EID: aab5473

Section: MW 10:30

Name: Sanjay Sivakumar

UT EID:

Section:

Checklist:

Part 1 -

- i. Simulation waveform of the Flight Attendant Call System for behavioral as well as dataflow modelling
- ii. K-map for minimizing the expression for next_state for dataflow modelling
- iii. Boolean expression for next_state for dataflow modelling
- iv. Completed design file (.v) for dataflow modelling

Part 2 -

- v. State Diagram of the Rising Edge Detector
- vi. Completed design files (.v) including the top module and clock divider
- vii. Test-bench of the system
- viii. Simulation waveform
- ix. Constraints File (Just the uncommented portion)

Part 3 -

- x. Completed design files (.v) of all the modules in the system
- xi. Test-bench of the system

- xii. Simulation waveform
- xiii. Constraints File (Just the uncommented portion)

Note → *The Verilog codes and the uncommented portions of the constraint files should be copied in your lab report and the **actual Verilog (.v), Constraint (.xdc) files and Bitstream (.bit) files** need to be zipped and submitted as well on Canvas. You are not allowed to change your codes after final submission as the TAs may download the submitted codes or bitstream files from Canvas during checkouts. For the truth Table, K-maps minimizations and algebraic expressions, you are free to draw them on paper and then put the pictures in your lab report, but please make sure it is legible for the TAs to grade it properly.*

Part 1:



`timescale 1ns / 1ps

```
module flight_attendant_call_system(
```

```
    input wire clk,
```

```
    input wire call_button,
```

```
    input wire cancel_button,
```

```
    output reg light_state
```

```
);
```

```
wire next_state;
```


```
assign next_state = (call_button) || (!(cancel_button) && light_state);
```

```
always @(posedge clk) begin
```

```
    light_state <= next_state;
```

```
end
```

```
endmodule
```

 


call	cancel	s	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

cancel/s	00	01	11	10
call	0	1	0	0
1	1	1	1	1

$$\text{next} = \text{call} + \text{cancel}'s$$

Part 2:

 

Verilog

```
`timescale 1ns / 1ps

module rising_edge_detector(

    input clk,

    input signal,

    input reset,

    output reg outedge

);

    wire slow_clk ;

    reg [1:0] state ;

    reg [1:0] next_state ;

    clkdiv cl(clk, reset, slow_clk);

    always @(*) begin

        case (state)

            2'b00 : begin

                outedge = 1'b0;

                if (~signal)

                    next_state = 2'b01;

                else
```

```

        next_state = 2'b00;

    end

    2'b01 : begin

        outedge = 1'b0;

        if (~signal)

            next_state = 2'b01;

        else

            next_state = 2'b10;

        end

    2'b10 : begin

        outedge = 1'b1;

        next_state = 2'b00;

        end

    default : begin

        next_state = 2'b00 ;

        outedge = 1'b0;

        end

    endcase

end

always @(posedge slow_clk) begin

    if (reset)

        state <= 1'b0;

    else

        state <= next_state;

    end

endmodule

Clock

`timescale 1ns / 1ps

module clkdiv(

    input clk,

    input reset,

    output clk_out

);

```

```

    reg [25:0] COUNT;

    assign clk_out = COUNT[25]

    always @(posedge clk)

    begin

    if ( reset )

        COUNT = 0;

    else

        COUNT = COUNT + 1;

    end

endmodule

Testbench

`timescale 1ns / 1ps

module tb_rising_edge_detector;

reg clk;

reg signal;

reg reset;

wire outedge;

rising_edge_detector u1 (

    .clk(clk),

    .signal(signal),

    .reset(reset),

    .outedge(outedge)

);

initial

begin

clk = 0;

reset = 0;

signal = 0;

```

```
#20;
```

```
signal = 0;
```

```
#20;
```

```
signal = 1;
```

```
#20;
```

```
signal = 1;
```

```
#20;
```

```
signal = 0;
```

```
#20;
```

```
signal = 1;
```

```
#20;
```

```
signal = 1;
```

```
#20;
```

```
signal = 0;
```


```
end
```

```
always
```

```
#10 clk = ~clk;
```

endmodule

Simulation

 

Constraints

```
set_property PACKAGE_PIN W5 [get_ports {clk}]

set_property IOSTANDARD LVCMOS33 [get_ports {clk}]

create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports {clk}]

set_property PACKAGE_PIN V17 [get_ports {signal}]

## Sets the switch to use 3.3V logic

set_property IOSTANDARD LVCMOS33 [get_ports {signal}]

set_property PACKAGE_PIN U18 [get_ports reset]

set_property IOSTANDARD LVCMOS33 [get_ports reset]

set_property PACKAGE_PIN U16 [get_ports {outedge}]

## Sets the LED to use 3.3V logic

set_property IOSTANDARD LVCMOS33 [get_ports {outedge}]
```


Part 3:

Verilog

```
`timescale 1ns / 1ps
```

```
module time_multiplexing_main(
```

```
    input clk,
```

```
    input reset,
```

```
    input [15:0] sw,
```

```
    output [3:0] an,
```

```
    output [6:0] sseg
```

```
);
```

```
    wire [6:0] in0, in1, in2, in3;
```

```
    wire slow_clk;
```

```
    hexto7segment c1 (.x(sw[3:0]), .r(in0));
```

```
    hexto7segment c2 (.x(sw[7:4]), .r(in1));
```

```
    hexto7segment c3 (.x(sw[11:8]), .r(in2));
```

```
    hexto7segment c4 (.x(sw[15:12]), .r(in3));
```

```
    clkdiv cl(clk, reset, slow_clk);
```

```
    time_mux_state_machine c6(
```

```
        .clk (clk),
```

```
        .reset (reset),
```

```
        .in0 (in0),
```

```
        .in1 (in1),
```

```
        .in2 (in2),
```

```
        .in3 (in3),
```

```
        .an (an),
```

```
        .sseg (sseg));
```

```
Endmodule
```

```

`timescale 1ns / 1ps

module time_mux_state_machine(

    input clk,

    input reset,

    input [6:0] in0,

    input [6:0] in1,

    input [6:0] in2,

    input [6:0] in3,

    output reg [3:0] an,

    output reg [6:0] sseg

);

    reg [1:0] state;
    reg [1:0] next_state;

    always @ (*) begin

        case(state)

            2'b00: next_state = 2'b01;

            2'b01: next_state = 2'b10;

            2'b10: next_state = 2'b11;

            2'b11: next_state = 2'b00;

        endcase

    end

    always @(*) begin

        case (state)

            2'b00 : sseg = in0;

            2'b01 : sseg = in1;

            2'b10 : sseg = in2;

            2'b11 : sseg = in3;

        endcase

        case (state)

```

```
        2'b00: an = 4'b1110;  
        2'b01: an = 4'b1101;  
        2'b10: an = 4'b1011;  
        2'b11: an = 4'b0111;  
  
    endcase  
  
end  
  
always @(posedge clk or posedge reset) begin  
  
    if(reset)  
  
        state <= 2'b00;  
  
    else  
  
        state <= next_state;  
  
    end  
  
endmodule
```

```
`timescale 1ns / 1ps  
  
module clkdiv(  
  
    input clk,  
  
    input reset,  
  
    output slow_clk  
  
);  
  
    reg [16:0] COUNT;  
  
    assign slow_clk = COUNT[16];  
  
    always @(posedge clk)  
  
    begin  
  
        if ( reset )  
  
            COUNT = 0;  
  
        else  
  
            COUNT = COUNT + 1;  
  
        end  
  
    endmodule
```

Testbench

```
`timescale 1ns / 1ps
```

```
module tb_time_multiplexing_main;
```

```
    reg clk;
```

```
    reg reset;
```

```
    reg [15:0] sw;
```

```
    wire [3:0] an;
```

```
    wire[6:0] sseg;
```

```
    time_multiplexing_main ul (
```

```
        .clk(clk),
```

```
        .reset(reset),
```

```
        .sw(sw),
```

```
        .an(an),
```

```
        .sseg(sseg)
```

```
    );
```

```
    initial
```

```
    begin
```

```
        clk = 0;
```

```
        reset = 0;
```

```
        sw = 0;
```

```
        #10;
```

```
        reset = 1;
```

```
        sw = 16'h0000;
```

```
        #10;
```

```
        sw = 16'h00A1;
```

```
        #10;
```

```
        sw = 16'h0B02;
```

```
        #10;
```

```
        sw = 16'hC003;
```

```

#10;

sw = 16'h00D4;

#10;


sw = 16'h0E05;

end

always #5 clk = ~clk;

endmodule

```

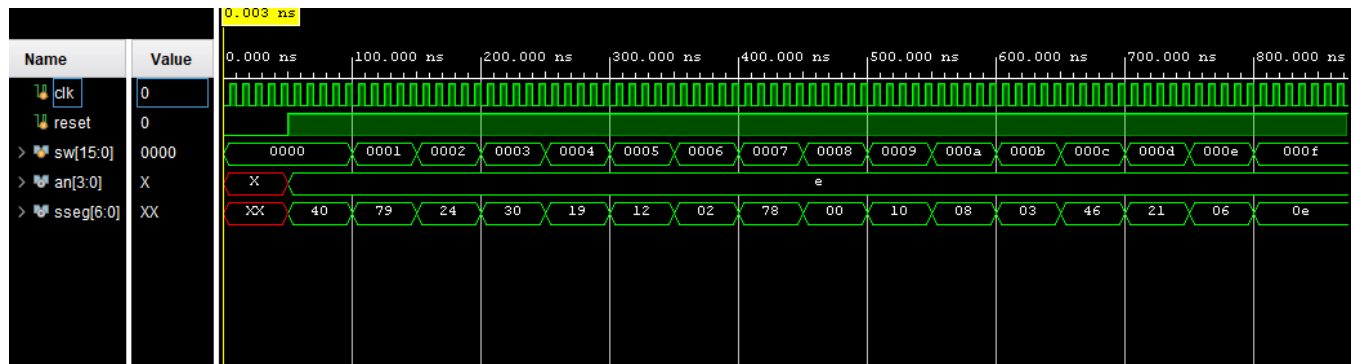

Constraints

```

set_property PACKAGE_PIN W5 [get_ports clk]

set_property IOSTANDARD LVCMOS33 [get_ports clk]

create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports clk]

set_property PACKAGE_PIN V17 [get_ports {sw[0]}]

## Sets the switch to use 3.3V logic

set_property IOSTANDARD LVCMOS33 [get_ports {sw[0]}]

## Connects pin V16 (SW1 on the board) to input b in our gate module

set_property PACKAGE_PIN V16 [get_ports {sw[1]}]

## Sets the switch to use 3.3V logic

set_property IOSTANDARD LVCMOS33 [get_ports {sw[1]}]

set_property PACKAGE_PIN W16 [get_ports {sw[2]}]

set_property IOSTANDARD LVCMOS33 [get_ports {sw[2]}]

set_property PACKAGE_PIN W17 [get_ports {sw[3]}]

set_property IOSTANDARD LVCMOS33 [get_ports {sw[3]}]

set_property PACKAGE_PIN W15 [get_ports {sw[4]}]

```

```
        set_property IOSTANDARD LVCMOS33 [get_ports {sw[4]]}

set_property PACKAGE_PIN V15 [get_ports {sw[5]]}

        set_property IOSTANDARD LVCMOS33 [get_ports {sw[5]]}

set_property PACKAGE_PIN W14 [get_ports {sw[6]]}

        set_property IOSTANDARD LVCMOS33 [get_ports {sw[6]]}

set_property PACKAGE_PIN W13 [get_ports {sw[7]]}

        set_property IOSTANDARD LVCMOS33 [get_ports {sw[7]]}

set_property PACKAGE_PIN V2 [get_ports {sw[8]]}

        set_property IOSTANDARD LVCMOS33 [get_ports {sw[8]]}

set_property PACKAGE_PIN T3 [get_ports {sw[9]]}

        set_property IOSTANDARD LVCMOS33 [get_ports {sw[9]]}

set_property PACKAGE_PIN T2 [get_ports {sw[10]]}

        set_property IOSTANDARD LVCMOS33 [get_ports {sw[10]]}

set_property PACKAGE_PIN R3 [get_ports {sw[11]]}

        set_property IOSTANDARD LVCMOS33 [get_ports {sw[11]]}

set_property PACKAGE_PIN W2 [get_ports {sw[12]]}

        set_property IOSTANDARD LVCMOS33 [get_ports {sw[12]]}

set_property PACKAGE_PIN U1 [get_ports {sw[13]]}

        set_property IOSTANDARD LVCMOS33 [get_ports {sw[13]]}

set_property PACKAGE_PIN T1 [get_ports {sw[14]]}

        set_property IOSTANDARD LVCMOS33 [get_ports {sw[14]]}

set_property PACKAGE_PIN R2 [get_ports {sw[15]]}

        set_property IOSTANDARD LVCMOS33 [get_ports {sw[15]]}
```

#7 segment display

```
set_property PACKAGE_PIN W7 [get_ports {sseg[0]]}

        set_property IOSTANDARD LVCMOS33 [get_ports {sseg[0]]}

set_property PACKAGE_PIN W6 [get_ports {sseg[1]]}

        set_property IOSTANDARD LVCMOS33 [get_ports {sseg[1]]}

set_property PACKAGE_PIN U8 [get_ports {sseg[2]]}

        set_property IOSTANDARD LVCMOS33 [get_ports {sseg[2]]}

set_property PACKAGE_PIN V8 [get_ports {sseg[3]]}

        set_property IOSTANDARD LVCMOS33 [get_ports {sseg[3]]}
```

```
set_property PACKAGE_PIN U5 [get_ports {sseg[4]]  
    set_property IOSTANDARD LVCMOS33 [get_ports {sseg[4]]  
set_property PACKAGE_PIN V5 [get_ports {sseg[5]]  
    set_property IOSTANDARD LVCMOS33 [get_ports {sseg[5]]  
set_property PACKAGE_PIN U7 [get_ports {sseg[6]]  
    set_property IOSTANDARD LVCMOS33 [get_ports {sseg[6]]
```

```
set_property PACKAGE_PIN U2 [get_ports {an[0]]  
    set_property IOSTANDARD LVCMOS33 [get_ports {an[0]]  
set_property PACKAGE_PIN U4 [get_ports {an[1]]  
    set_property IOSTANDARD LVCMOS33 [get_ports {an[1]]  
set_property PACKAGE_PIN V4 [get_ports {an[2]]  
    set_property IOSTANDARD LVCMOS33 [get_ports {an[2]]  
set_property PACKAGE_PIN W4 [get_ports {an[3]]  
    set_property IOSTANDARD LVCMOS33 [get_ports {an[3]]
```

#Buttons

```
set_property PACKAGE_PIN U18 [get_ports reset]  
    set_property IOSTANDARD LVCMOS33 [get_ports reset]
```